



Page NO.

1. 1 to 29 – Mid Term
2. 30 to 66- Final Term

MD IFTAKHAR KABIR SAKUR

25th BATCH

COMPUTER AND COMMUNICATION ENGINEERING

International Islamic University Chittagong

COURSE CODE: CCE-4707

COURSE TITLE: Microwave Engineering

COURSE TEACHER:

[Md Mostafa Amir Faisal](#)

Assistant Professor

ETE

MW Frequency

⇒ Radio Frequency (RF) & MW Engineering
Covers AC signals with frequencies in the
range of 100 MHz to 1000 GHz

Transmission Line

Generator থেকে Load পর্যন্ত power কে নিয়ে
যাওয়া কাজ মে করে তাকে transmission Line
বলে

⇒ The thing which takes power from generator
to load is called as transmission line.

Why Transmission Line Theory:

→ A transmission line is a two conductor
system, where one is used to send
forward current & the other one is
used for bringing return current.

→ The key difference between a circuit
theory & Transmission Line Theory is in

their electrical size.

Circuit Analysis assumes that the physical dimensions of the networks are much smaller than the electrical wavelength.

And a transmission lines are many wavelength in size.

For Example For a 50000 MHz signal the wavelength is 10 km then we will

have to use transmission line theory instead of circuit theory.

DIF * In circuit theory we assume that the magnitude phase ~~are~~ can't vary

And we also assume that in transmission line theory magnitude phase can be varied.

DIF * circuit If the circuit length is near to wavelength then we will use Transmission Line Theory

on the other hand, if the electrical length is much smaller than the wavelength then the ~~to~~ circuit theory will be used.

note:- (i) current grow from magnetic field
(ii) voltage grow from electrical field.

⇒ An ordinary electrical cable suffice to carry low frequency AC such as main power which reverses direction 100 to 120 times per second. However, they can't be used to carry currents in the radio frequency range above 30 kHz cause the energy tends to radiate off the cable as radio waves, causing power losses.

So to get rid of this radiation loss two conductors are used & arranged that their electromagnetic fields are in opposite direction.

To meet this requirement, the current of conductor must flow in opposite direction

that means shifted by π in phase
by 180 degrees.

3 types of theory -

Circuit

Brief

① Why Transmission Lines should be parallel?

Why two conductors are needed & closed together?

parallel:-

to get rid of this radiation loss two conductors are used & arranged that their electromagnetic fields are in opposite direction. To meet the requirement the current of conductors must flow in opposite direction.

Q. Why

Two conductors are needed & closed?

Generator or power or Load, पार्श्व निष्ठा माध्यम

এই কাজ মে করে আক Transmission Line, কাল।

we need: -


→ Two conductors:

- 1) One conductor will take forward current
- 2) Another one will take bring return current.

→ Two conductors will be in parallel &

→ Two conductors are very close to each other.

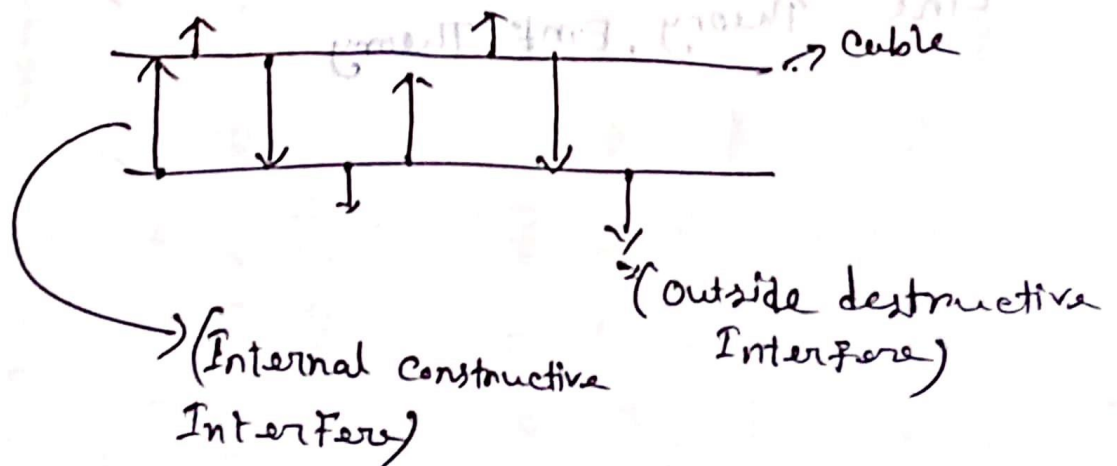So that the angle of path difference can't be changed.



VSM

- How many conditions are needed for TL or
- When to use Transmission Line theory or
- Why Transmission Line Theory is used?

Ans: -


① \rightarrow If the wavelength for 50,000 MHz signal is 10 km then we need to use Transmission Line Theory instead of circuit theory

② \rightarrow In circuit theory we assume that magnitude and phase can't vary

But, in transmission line theory it can be varied.

③ \rightarrow When circuit length is almost equal to wavelength then Transmission Line Theory is used.

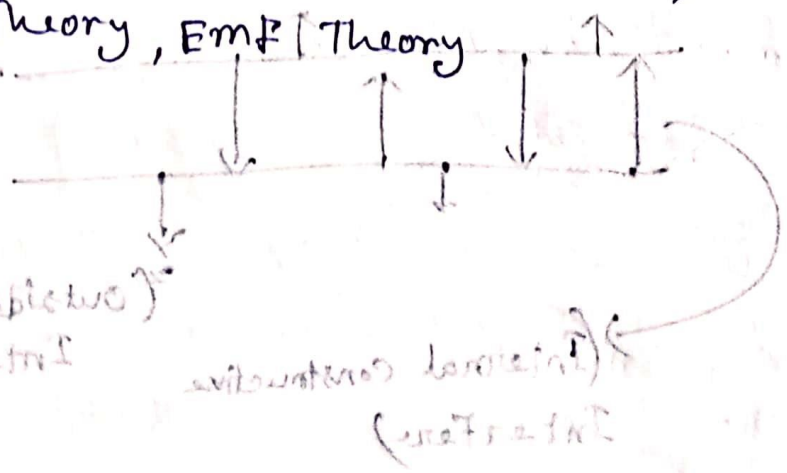③ Discussion on circuit theory, Transmission Line Theory, EMF Theory



How many conditions are needed for TL or when to use Transmission Line Theory or why Transmission Line Theory is used?


If the wave length for 50,000 MHz signal is 10 km then we need to use Transmission Theory instead of circuit Theory.

In circuit Theory we assume that magnitudes are don't vary.

In transmission line Theory it can be used.



When circuit length is almost equal to wave length then Transmission Line Theory is used.

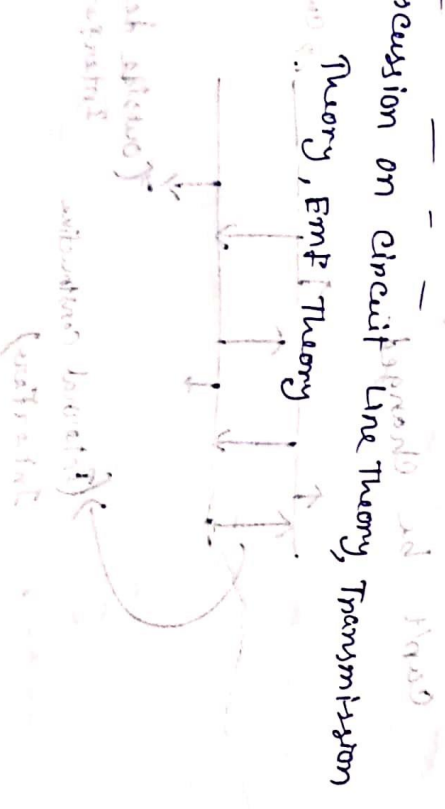Discussion on circuit Line Theory, Transmission Theory, EMP Theory



Transmission Line	Circuit Line	EMF
① Crucial For High Frequency long distance signal transmission	① Connected components like resistors, capacitors & IC etc on PCB.	① For Electromotive Force, is a fundamental concept.
② Consist of two conductors that carry electrical signals between two points.	② Lines facilitates the flow of current between components & enabling the circuit to perform its intended function.	② EMF are consisted with battery, generator in circuit.
③ Can be thought distributed circuits, where the interaction between capacitance, inductance & resistance & impedance are important.	③ The width, thickness, & material of these lines impact their resistance, capacitance & other electrical characteristics.	③ It's the energy driving the electric charges to move through a circuit.
④ Key parameters include characteristic impedance, propagation delay, reflection coefficient.	④ Design consideration for circuit lines include minimizing resistance, managing impedance & avoiding signal interference	④ It is not a force in the mechanical sense. It's a measure of energy conversion.

Equivalent circuit representation of TL

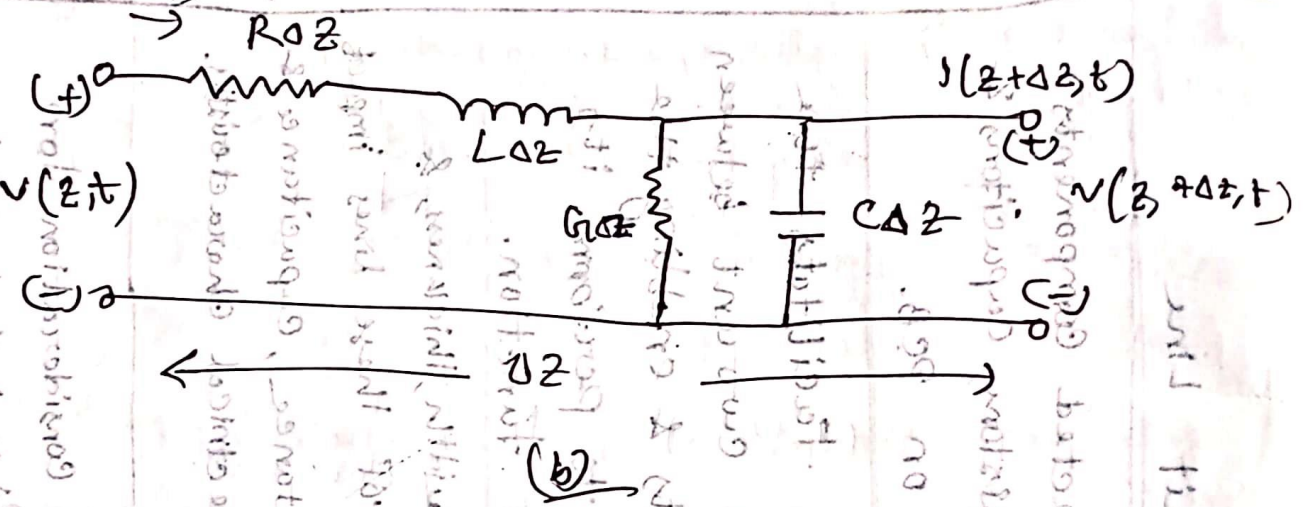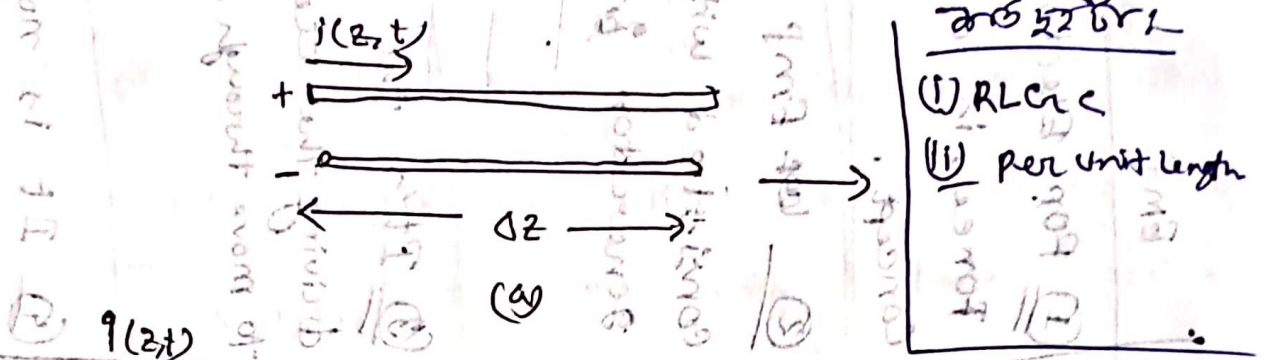

⇒ In the figure a transmission line is schematically represented as a two-wire line since transmission lines (for transverse electromagnetic [TEM] wave propagation) always have at least two conductors.

- Four fundamental parameters:
- R = Series resistance per unit length, for both conductors (Ω/m)
 - L = Series inductance per unit length, for both conductors, in H/m

(VSWR)

60x
60

100 + j150 \rightarrow 50 lossless line $\rightarrow \frac{100 + j150}{50} = 2 + 3j$ $\begin{matrix} \nearrow \text{resistance} \\ \searrow \text{reactive} \end{matrix}$

(1) Reflection coefficient, $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{2 + 3j - 50}{2 + 3j + 50} = \frac{-48 + 3j}{52 + 3j}$

(2) $S(VSWR) = \frac{1 + |\Gamma|^2}{1 - |\Gamma|^2} = \frac{1 + 0.747^2}{1 - 0.747^2} = 7$

(3) Load Admittance, $Y_L = \frac{1}{Z_L} = \frac{1}{2 + j3} = \frac{2 - j3}{2^2 + 3^2} = \frac{2 - j3}{13}$

(4) Z_{in} at 0.4 λ from the load. $Z_{in} = \frac{0.154 - 0.231j}{50} = 0.00308 - 0.00462j$

$\Rightarrow 0.213 + 0.4 \lambda$

$= 0.613 \lambda$

$\therefore Z_{in} = (0.24 + j0.81) \times 50$

$= (0.24 + j0.81) \times 50$

$= 12 + 40.5j \Omega$

(5) The V_{max} & V_{min} with respect to the load if the line is 0.6 λ long.

\Rightarrow 0.6 λ distance from load

$0.6 \lambda + 0.213 = 0.813$

Now, 1st $V_{max} = (0.25 - 0.213) = 0.037$

(Answer)

$$\text{2nd part } v_{\text{max}} = (0.037 + 0.5) \lambda$$

$$\frac{5.375}{0.8} = v_{\text{max}} = 0.537 \lambda$$

$$v_{\text{min}} = (1st \text{ part } v_{\text{max}} + 0.25) \lambda$$

$$= 0.037 + 0.25$$

$$= 0.287$$

⊛ What is propagation constant? And how does it give info about wave?

⇒ Propagation constant is denoted by γ .

It describe the behavior of electromagnetic waves or other types of propagating waves as they travel through a medium.

It has two parts:-

① Attenuation constant (α):-

This part describe the exponential decay of the wave's amplitude as it travel through medium. And also describe how much the wave's energy is lost per unit length due to absorption or scattering.

A higher value of α indicates greater attenuation.

(2) Phase constant (β): - How much the phase of the

wave changes as it propagates through the medium. It indicates the phase shift experienced by the wave per unit length of propagation. It determines wave's spatial variation along the propagation direction.

$$\gamma = \alpha + i\beta \quad | \quad i = \text{imaginary number}$$

→ Here α is responsible for attenuation of the wave's intensity, while β is responsible for the phase shift. And together they provide information about how the wave's amplitude decreases and how its phase evolves as it travels through the medium.

$$\frac{\sqrt{R + i\omega L}}{\sqrt{G + i\omega C}} = \dots$$

Q. What is 'lossless' line? Justify the assumption

of MW Transmission Lines as lossless lines?

⇒ A Lossless Line:

It is a theoretical type of transmission line that has no resistance, conductance, dielectric loss. In other words, it is a transmission line that has zero losses and can transmit signals without any power loss.

⇒ A low loss line is possible when,

$$R \ll \omega L \quad \& \quad G \ll \omega C$$

So, we can find,

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$= j\omega \sqrt{LC}$$

$$\text{or, } \beta = \omega \sqrt{LC}, \quad \alpha = 0$$

The attenuation, $\alpha = 0$

$$\text{Characteristic impedance, } Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$
$$= \sqrt{\frac{L}{C}}$$

$$I = \frac{V}{Z_0}$$

Now, it is a real number. So the ~~soln~~ general solution of,

$V(z) =$
Lossless Transmission Line (voltage)

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$$


$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z}$$

Waves

Angular frequency, phase constant, phase velocity:

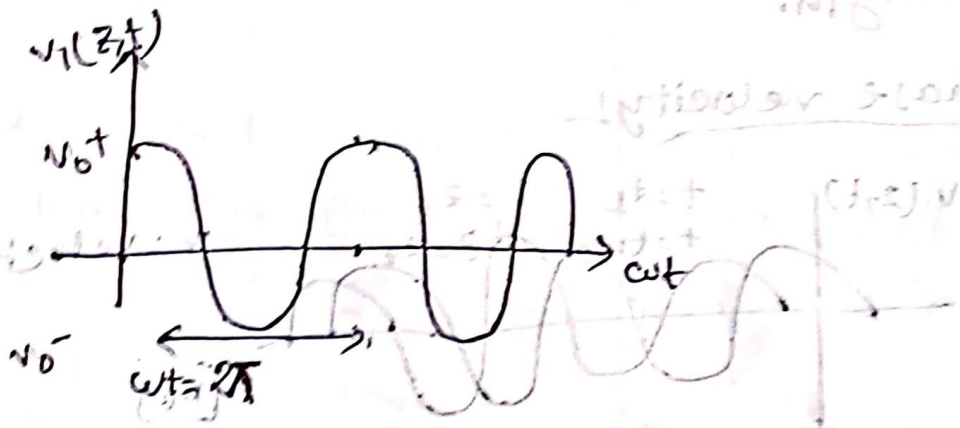(i) Angular Frequency:


$$V_1(z,t) = V_0^+ \cos(\omega t - \beta z)$$



$$\omega t = 2\pi$$

$$\Rightarrow T = \frac{2\pi}{\omega} = \frac{1}{f} \quad [T = \text{Time period of wave}]$$

(i) Phase constant

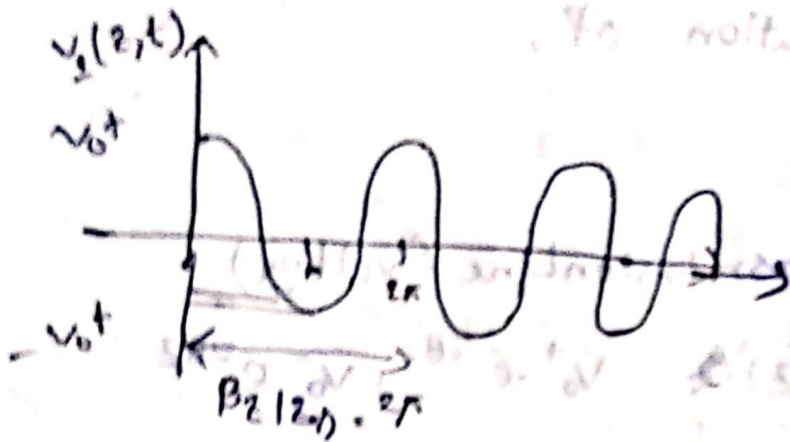


$$\beta z | z=\delta = 2\pi$$

$$\Rightarrow \delta = \frac{2\pi}{\beta} \quad |\delta = \text{wavelength}|$$

Distance between two consecutive equal values of the signal is defined as the wavelength.

(ii) Phase velocity

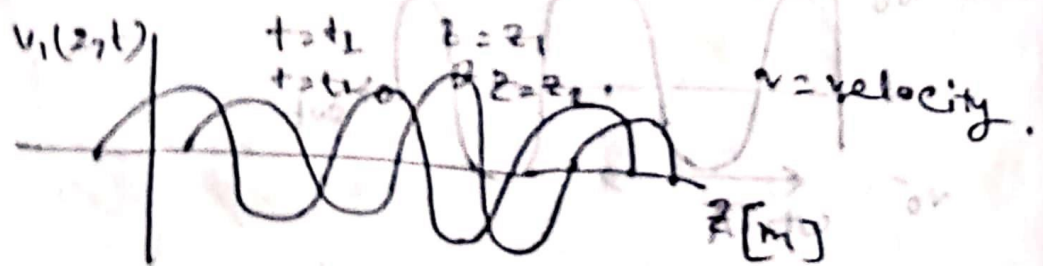

$$v_1(z_1, t_1) = v_2(z_2, t_2)$$

$$\Rightarrow \cos(\beta z_1 - \omega t_1) = \cos(\beta z_2 - \omega t_2)$$

$$\Rightarrow \frac{z_2 - z_1}{t_2 - t_1} = \frac{\omega}{\beta} \Leftarrow \beta z_1 - \omega t_1 = \beta z_2 - \omega t_2$$

$$\Rightarrow v_p = \frac{c}{\beta} = \frac{w}{\omega\sqrt{Lc}} = \frac{1}{\sqrt{Lc}}$$

$$\text{So, wavelength, } \lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega\sqrt{Lc}} = \frac{v_p}{f} = \lambda_{pt}$$

⊛ Difference between characteristic impedance & Line impedance.

⇒

Characteristic Impedance

① Related to the physical quantities & Frequency of the transmission line. Reflected voltage, current waves.

② Important params to calculate line params & calculate impedance.

③ Helps to determine params of TL.

Line Impedance

① varies as we go distance from load to source. Characteristic Impedance doesn't vary.

② New combined total impedance seen at a distance from load.

③ Helps to determine impedance

Converting a Transmission Line into an Arbitrary Load. Then what will

be the reflection coefficient?

⇒ Converting a transmission line into an arbitrary load involves terminating the

transmission line with an impedance that are not necessarily matched to the characteristic impedance of transmission line.

The reflection coefficient $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$

Z_L = Load impedance

Z_0 = The characteristic impedance of TL

When $Z_L = Z_0$ then $\Gamma = 0$

When Z_L is not equal to Z_0 then Γ is non zero

So, if converted into arbitrary load & not matched to characteristic impedance of the TL, the reflection coefficient will be non-zero. That means there will be some amount of signal reflection at the load interface.

Q1 Difference between Return Loss, VSWR, Insertion Loss

Return Loss	VSWR	Insertion Loss
<p>1) Measure of the amount of signal power that is reflected back towards the source due to impedance mismatch.</p>	<p>1) Measure of how well the load is matched to the transmission line's characteristic impedance. It is a ratio</p>	<p>1) Reduction of signal power when a device or component is inserted into a transmission line or network.</p>
<p>2) Expressed in dB</p>	<p>2) Ratio of maximum voltage along the transmission line</p>	<p>2) used to quantify the signal attenuation caused by the insertion of the device.</p>
<p>3) $RL = -20 \cdot \log_{10}(\Gamma)$</p>	<p>3) $VSWR = \frac{1 + \Gamma }{1 - \Gamma }$</p>	<p>3) $IL = P_{in} - P_{out}$</p>
<p>4) Higher return loss value indicates less signal reflection & better impedance match. A perfect match results in infinite return loss.</p>	<p>4) A lower VSWR (closer to 1) indicates better impedance matching.</p>	<p>4) Higher Insertion Loss indicates greater signal attenuation caused by the insertion of the component.</p>

Q1 Calculate ^{or} write down the formulas for
 Line impedance & Input impedance which are
 from L distance from Load of transmission.

⇒ Considering a lossless transmission line

And characteristic impedance (Z_0) propagation

constant (β), Z_L = Load impedance, Z_{in} = Input impedance.

So, equation for line impedance from Distance L

From Load:-

$$Z_L = Z_0 \frac{Z_{in} + j Z_0 \tan(\beta L)}{Z_0 + j Z_{in} \tan(\beta L)}$$

Input Impedance (Z_{in}) from Distance L:-

$$Z_{in} = Z_L \frac{Z_0 + j Z_{in} \tan(\beta L)}{Z_{in} + j Z_0 \tan(\beta L)}$$

Q2 Derive the equations for Line Impedance

Reflection coefficient & Telegrapher's equation.

⇒ Line Impedance:-

$$I(z) = \frac{V(z)}{Z_0} e^{-j\beta z} - \frac{V(z)}{Z_0} e^{j\beta z}$$

$$\text{Voltage } V(0) = V_{load}$$

$$\therefore I_{load} = \frac{V_{load}}{Z_0} + \frac{V}{Z_0}$$

Solving for V^- & substituting the definition of


no waves are reflected

$$V^- = \frac{Z_L - Z_0}{Z_L + Z_0} V^+$$

Can be found if we know Z_L and Z_0
 [Telegrapher & reflection coefficient previous]

~~Quarter wavelength transformer~~ what is
 (iii) What is a quarter wavelength transformer?
 What is the condition of achieving impedance matching with it?

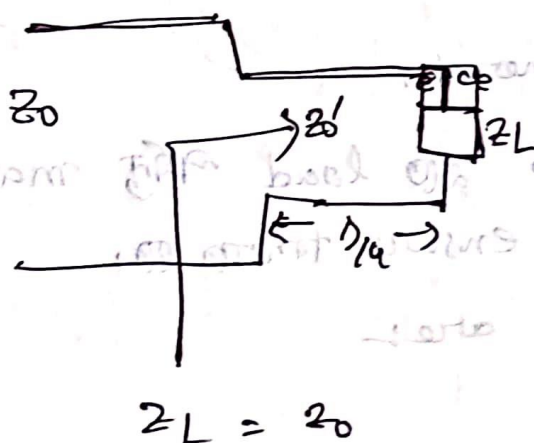⇒ The $\lambda/4$ section of the transmission line is called quarter-wave length cause it is used for impedance matching like on ordinary transformer.



When $Z_0 \neq Z_L$ that means load is mismatched and a reflected wave exists on the line. The maximum power transfer

can be gained when it is matched.

For that $Z_0 = Z_L$ so that there is no reflection.

$$\Rightarrow Z_{in} = Z_0 \left[\frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right] = \frac{Z_0^2}{Z_L} \quad \text{--- (i)}$$

$$\Rightarrow \frac{Z_{in}}{Z_0} = \frac{Z_0}{Z_L} \quad \text{--- (ii)}$$

$$\Rightarrow Z_{in} = \frac{1}{Z_L} \quad \text{--- (iii)}$$

From (i) Z_0 is selected such that $(Z_{in} = Z_0)$

$$Z_0 = \sqrt{Z_0 Z_L} \quad [Z_0, Z_0, Z_L \text{ are real}]$$

$Z_L =$ Load impedance

$Z_0 =$ Line "

$Z_G =$ Generator "

For Generator Z_G load Z_L max power transfer Z_G or ensure $Z_G = Z_L$

Ans:- Conditions are:-

(i) $Z_0 = Z_L$

(ii) $Z_G = Z_{in}$

① Load & Generator Impedances are 73Ω & 50Ω respectively, Design a quarter wavelength transformer for proper impedance matching between them.

$$S = \frac{P_{out}}{P_{in}} = \frac{S}{1} = 1$$

⇒ To design quarter wavelength,

we need characteristic impedance, $Z_0 = \sqrt{Z_L \times Z_S}$

$$= \sqrt{73 \times 50}$$

$$= 60.62\Omega$$

Now, determining the electrical length of the quarter wavelength,

$$BL = \left(\frac{\pi}{2}\right)$$

$B =$ phase constant

$L =$ electrical length

The phase constant can be calculated:-

$B = \frac{2\pi}{\lambda}$

$\lambda =$ wavelength of Transmission Line.

$$\lambda = 4L$$

$$B \cdot \text{value} \Rightarrow \frac{2\pi}{\lambda} \times L = \frac{\pi}{2}$$

$$L = \frac{c}{4f\sqrt{\epsilon_r}}$$

Assuming that transmission line to be air filled,

$\epsilon_r = 1$, plug in the given freq. of 2.4 GHz

We get

$$L = \frac{c}{4f} = \frac{3 \times 10^8}{4 \times 2.4 \times 10^9} = 31.25 \text{ mm}$$

So the electrical length of the quarter wavelength transformer is 31.25 mm.

Lecture - 5

Q1

Difference between TL & waveguide.

Q1 =>

Transmission Line	Waveguide
① Two separated conductors in parallel.	① Single conductor
② For low power transmission	② For bulk power transmission.
③ TEM Mode	③ TE/TM Mode
④ Works for any frequency generally.	④ Works like a high pass filter.

Q2

Difference between TEM, TM, TE

TEM	TM	TE
① Transverse Electro magnetic wave	① Transverse magnetic	① Transverse Electric
② $E(z) = 0$	② $E(z) \neq 0$	② $E(z) \neq 0$
③ $H(z) = 0$	③ $H(z) = 0$	③ $H(z) \neq 0$
④ Doesn't have a cut off frequency.	④ Has a cut off frequency.	④ Has a cut off frequency.

VVI

Procedure for analyzing TEM

(1) Solving Laplace equation $\nabla^2 \phi(x,y) = 0$,

For $\phi(x,y)$. The solution will contain several unknown constants,

(2) Find these constants by applying the boundary

conditions for the known voltages on the conductors,

(3) Compute \bar{e} & \bar{E} . Compute \bar{h} & \bar{H} .

(4) Compute V & I .

(5) The propagation constant is given by $\beta = \omega \sqrt{\mu \epsilon} = k$

and the characteristic impedance is

given by $Z_0 = V/I$.

VVI

Procedure for TM & TE

(1) Solve the reduced Helmholtz equation for h_z or

e_z . The solution will contain several unknown

constants & the unknown cutoff wave number, k_c .

(2) By using,

$$E_y = \frac{j\omega \mu}{k_c^2} \cdot \frac{dH_z}{dx} \quad \text{--- (1)}$$

And also, using this equation find the transverse fields from h_z or e_z .

(3) Apply the boundary conditions to the appropriate field components to find the

unknown constant & k_c

(4) The propagation constant is given by

$$k_c^2 = k^2 - \beta^2$$

And the characteristic impedance is given by $Z_0 = \sqrt{\mu/\epsilon}$.

Parallel plate waveguide:

$$\beta = \sqrt{k^2 - k_c^2}$$

$$= \sqrt{k^2 - (n\pi/a)^2}$$

Observe that for $n=0$, $\beta = k = \omega\sqrt{\mu\epsilon}$ and that $B_z = 0$. The E_y & H_x fields are then constant in

From this equation we can see that

β is real only when $k > k_c$. Because $k = \omega\sqrt{\mu\epsilon}$

$k = \omega\sqrt{\mu\epsilon}$ is proportional to frequency, the TM_n

modes for $(n > 0)$ exhibit a cut off frequency of the TM_n mode can be found as,

$$f_{cutoff} = \frac{kc}{2\pi\sqrt{\mu\epsilon}} = \frac{nc}{2d\sqrt{\mu\epsilon}}$$

Rectangular wave guide:

Dominant Mode of Frequency:

Wave guide of TE characteristic type

→ TE_{10} mode dominant TE mode. And the overall dominant mode of the rectangular waveguide.

→ TE_{11} mode dominant mode of circular waveguide.

→ TE_{01} mode to lower order propagating mode.

→ TM_0 , Dominant mode of dielectric slab waveguide.

$k = \omega\sqrt{\mu\epsilon}$ is proportional to frequency. The TM_0 is lowest only when $k > k_c$. Because k_c is constant for a given waveguide.

~~75~~ 73Ω & 50Ω

$$Z_L = \sqrt{73 \times 50}$$

$$= 60.42 \Omega$$

Electrical length of quarter wavelength

$$\beta L = \frac{\pi}{2} \quad \left| \begin{array}{l} \beta = \text{phase const.} \\ L = \text{Length} \end{array} \right.$$

The phase constant can be calculated,

$$\beta = \frac{2\pi}{\lambda}$$

$$L = \frac{\pi}{2}$$

$$L = \frac{c}{4f\sqrt{\epsilon_p}} = \frac{c}{4f}$$

Here, in air $\epsilon_p = 1$ so, $L = \frac{c}{4f}$

plugging in the given freq, 2.4 GHz

$$L = \frac{3 \times 10^8}{4 \times 2.4 \times 10^9} = 31.25 \text{ m}$$

(i) $(R + j\omega L) \cdot I(s) = V(s)$

(ii) $(R + j\omega L) \cdot I(s) = \frac{V(s)}{s}$

Differentiating in both sides

(i) $\frac{d}{dt} (R + j\omega L) \cdot I(s) = \frac{d}{dt} V(s)$

(ii) $\frac{d}{dt} (R + j\omega L) \cdot I(s) = \frac{d}{dt} \left(\frac{V(s)}{s} \right)$

practice

KVL:

$$V(z, t) + V(z + \Delta z, t)$$

$$= R \Delta z I(z, t) + L \Delta z \frac{\partial I(z, t)}{\partial t}$$

$$= V(z, t) - V(z - \Delta z, t)$$

$$= R I(z, t) - L \frac{\partial I(z, t)}{\partial t}$$

$$\therefore -\frac{\partial V(z, t)}{\partial z} = R I(z, t) + L \frac{\partial I(z, t)}{\partial t} \quad [\Delta z \rightarrow 0]$$

KCL

$$I(z, t) - I(z + \Delta z, t)$$

$$= G \Delta z V(z, t) + C \Delta z \frac{\partial V(z, t)}{\partial t}$$

$$\therefore \frac{\partial I(z, t)}{\partial z} = -G V(z, t) - C \frac{\partial V(z, t)}{\partial t} \quad [\Delta z \rightarrow 0]$$

Telegrapher's wave eqn

$$\frac{dV(z)}{dz} = -(R + j\omega L) \cdot I(z) \quad \text{--- (i)}$$

$$\frac{d(I(z))}{dz} = -(G + j\omega C) \cdot V(z) \quad \text{--- (ii)}$$

Differentiating in both way we get,

$$\text{(i)} \quad \frac{d^2 V(z)}{dz^2} - \gamma^2 V(z) = 0$$

$$\text{(ii)} \quad \frac{d^2 I(z)}{dz^2} - \gamma^2 I(z) = 0$$

practice

Lossless Transmission

$$R \ll \omega L \quad G \ll \omega C$$

$$\gamma = \alpha + j\beta$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$= \sqrt{j\omega LC}$$

$$= j\omega \sqrt{LC}$$

$$\beta = \omega \sqrt{LC}, \quad \alpha = 0$$

Characteristic impedance, $Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$

Lossless Transmission, $Z_0 = \sqrt{\frac{j\omega L}{j\omega C}} = \sqrt{\frac{L}{C}}$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} + \frac{V_0^-}{Z_0} e^{j\beta z}$$

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$$



**KEEP
CALM
ITS TIME FOR THE
FINAL
EXAM**

Network Analysis

TE Mode:- Transverse Electric Mode in the context of waveguide propagation. & electromagnetic field analysis. In this mode, the electric field vector is perpendicular to the direction of wave propagation.

It implies that there is no electric field component parallel to the direction of wave propagation.

In TE E_z = 0, H_z != 0

TEM Mode:- Transverse Electromagnetic Mode.

Both the electric field & the magnetic field are perpendicular to the direction of propagation.

In this mode, there is no electric or magnetic field in the direction of propagation.

~~E_z != 0, H_z = 0~~
E_z = 0, H_z = 0

TM Mode! - Transverse Magnetic Mode, is a type of electromagnetic wave propagation in which the magnetic field is perpendicular with wave propagation.

And there is no electric field in this direction of propagation.

$$E_z \neq 0 \quad H_z = 0$$

As in TE & TM Mode, they don't have two terminal voltage & current measure can't happen in these.

But TEM mode as it has two terminal we can easily measure voltage & current from Laplace equation.

So, to get Impedance in TE & TM mode we need to find measure equivalence current on equivalence voltage.

⊗ For microwave network analysis we need to know the impedance at every point.

In TEM Mode as we directly measure voltage & current

$$V = \oint E \cdot dl$$

$$I = \oint H \cdot dl$$

For TE & TM Mode:-

To measure equivalent current & equivalent voltage some consideration is needed:-

① voltage of Transverse electric field and current of Transverse magnetic field

② The equivalent voltage & currents should be defined so that their product gives the power

③ The ratio of the voltage & current should be equal to the characteristic impedance of the line.

Various types of Impedance

1] Intrinsic Impedance:- This impedance is dependent only on the material parameters of the medium and is equal to the wave impedance for the plane or TEM mode wave.

That means,

$$Z_{TEM} = \eta_0$$

2] Wave impedance:- The measure of the opposition that an electromagnetic wave encounters as it propagates through a medium.

$$Z_{TE} = \frac{E}{H}$$


(iii) Characteristic Impedance:

Ratio of voltage to current for a travelling wave on a transmission line.

$$I_0 = \frac{V^+}{Z_0}$$

Impedance & Admittance matrices


There are n th ports.

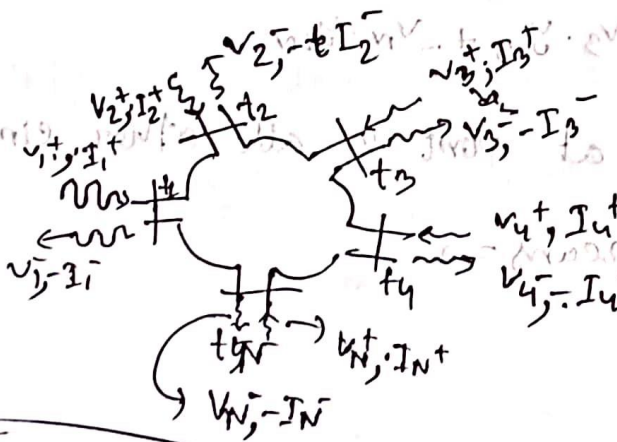

At the n th terminal plane, the total voltage & current is,

$$V_n = V_n^+ + V_n^- \quad \text{--- (1)}$$
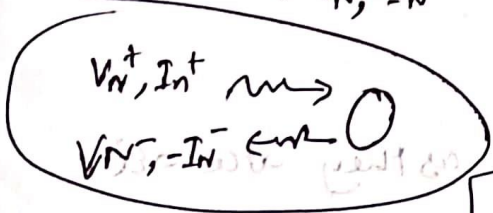
$$I_n = I_n^+ - I_n^- \quad \text{--- (2)}$$



S-matrices (Scattering matrices)

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ \vdots \\ V_n \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & Z_{13} & \dots & Z_{1n} \\ Z_{21} & Z_{22} & Z_{23} & \dots & Z_{2n} \\ Z_{31} & Z_{32} & Z_{33} & \dots & Z_{3n} \\ \vdots & \vdots & \vdots & \ddots & \vdots \\ Z_{n1} & Z_{n2} & Z_{n3} & \dots & Z_{nn} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_n \end{bmatrix}$$

$[V] = [Z][I]$ From this matrix = $V_1 = I_1 Z_{11} + I_2 Z_{12} + \dots + I_N Z_{1N}$

So, we know,

So, $Z_{12} = \frac{V_1}{I_2} \Big|_{I_1, I_3, \dots, I_N = 0}$ (iii)
 $I_1, I_3, \dots, I_N = \text{open circuit} = 0$

$V = I \cdot Z$

$V = I \cdot \frac{1}{Y}$

$I = Y \cdot V$

$$\begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_N \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} & y_{13} & \dots & y_{1N} \\ \vdots & \vdots & \vdots & \ddots & \vdots \\ y_{N1} & y_{N2} & y_{N3} & \dots & y_{NN} \end{bmatrix} \begin{bmatrix} V_1 \\ \vdots \\ V_N \end{bmatrix}$$

$\Rightarrow [I] = [Y][V]$

From here

$I_1 = V_1 \cdot y_{11} + V_2 \cdot y_{12} + V_3 \cdot y_{13} + \dots + V_N \cdot y_{1N}$

So, if I give current at port 2, all other circuit will be open, that means = 0

So,

$I_1 = V_2 \cdot y_{12}$

$y_{12} = \frac{I_1}{V_2} \Big|_{V_1, V_3, V_4, \dots, V_N = 0}$ as they are all 0

Note: - But if we have 10 port devices, there will be 100 of parameters, which are unknown. As a result we need to use some techniques.

⊛ Reciprocal Network!

Z_{13} & Z_{31}

Z_{13} means \rightarrow Giving input current at port 3 &

Z_{31} means \rightarrow (i) Getting output at port 1 (voltage)

$Z_{31} \rightarrow$ port - 1 = current input

port - 3 = measure output voltage.

So, if we get such microwave device in which the path in between two path are same, then we can say that, $Z_{13} = Z_{31}$

This is called reciprocal.

⊛ Lossless line! If the resistance $R=0$


That means, $Z = R + j\omega L$

$= 0 + j\omega L$

$[Z = j\omega L]$

⊛ Scattering matrix!

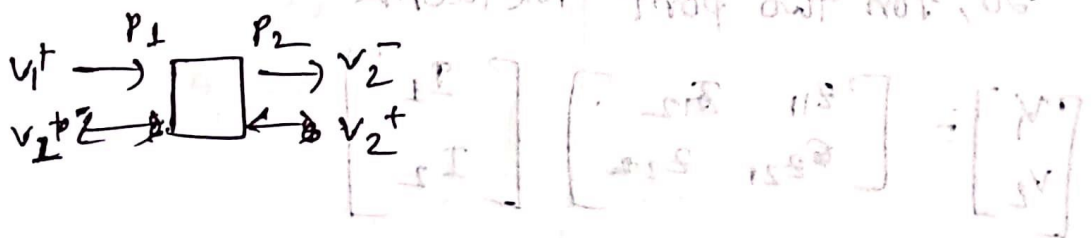Forward voltage (v^+) & Reflected voltage (v^-)



S matrix

$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

$$V_1^- = S_{11} V_1^+ + S_{12} V_2^+ \quad \text{--- (i)}$$

$$V_2^- = S_{21} V_1^+ + S_{22} V_2^+ \quad \text{--- (ii)}$$


$$S_{11} = \frac{V_1^-}{V_1^+} \Big|_{V_2^+ = 0} \quad S_{21} = \frac{V_2^-}{V_1^+} \Big|_{V_2^+ = 0}$$

$$S_{12} = \frac{V_1^-}{V_2^+} \Big|_{V_1^+ = 0} \quad S_{22} = \frac{V_2^-}{V_2^+} \Big|_{V_1^+ = 0}$$

Example

Find the Z parameter of the two port of

T-Network:

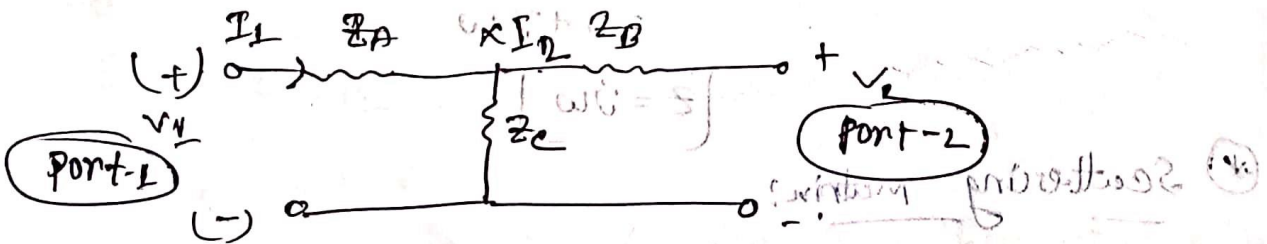

So, for two port Network

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$z_{11} =$$

$$v_1 = z_{11} \cdot I_1 + z_{12} \cdot I_2$$

$$v_2 = z_{21} \cdot I_1 + z_{22} \cdot I_2$$

$$z_{11} = \frac{v_1}{I_1} \Big|_{I_2=0}$$

$$z_{12} = \frac{v_1}{I_2} \Big|_{I_1=0}$$

$$z_{21} = \frac{v_2}{I_1} \Big|_{I_2=0}$$

$$z_{22} = \frac{v_2}{I_2} \Big|_{I_1=0}$$

So, z_A

So, for z_{11}

$$v_1 = z_{11} \cdot I_1 (z_A + z_c)$$

$$\Rightarrow z_{11} = \frac{v_1}{I_1} (z_A + z_c)$$

$$\Rightarrow z_{11} =$$

$$v_1 = I_1 (z_A + z_c)$$

$$\Rightarrow z_{11} \cdot I_1 = I_1 (z_A + z_c)$$

$$\Rightarrow z_{11} = \frac{I_1 (z_A + z_c)}{I_1}$$

$$\Rightarrow z_{11} = z_A + z_c$$

For, z_{12}

$$v_1 = z_{12} \cdot I_2 \Big|_{I_1=0}$$


$$v_1 = I_2 \cdot z_c$$



$$z_{12} = \frac{I_2 z_c}{I_2}$$

$$z_{12} = z_c$$

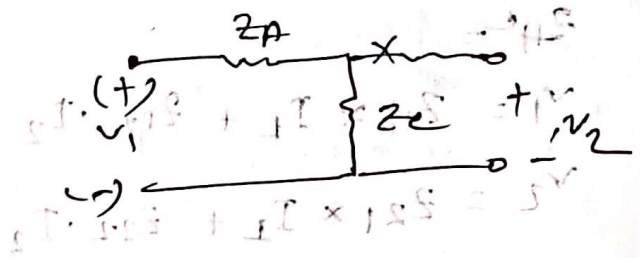For, $Z_{21} = \frac{V_2}{I_1} \mid I_2 = 0$



$V_2 = I_1 \cdot Z_{21}$

$Z_{21} = \frac{I_1 \cdot Z_C}{I_1} = Z_C$

$Z_{21} = Z_C$

For, $Z_{22} = \frac{V_2}{I_2} \mid I_1 = 0$

$Z_{22} = \frac{I_2 (Z_B + Z_C)}{I_2}$

$\frac{V}{I} = 11 \Omega = Z_B + Z_C$

$5 \Omega + Z_C = 11 \Omega$



$5 \Omega + Z_C = 11 \Omega$

$Z_C = 6 \Omega$

$(5 \Omega + 6 \Omega) I = 11 V$

$(5 \Omega + 6 \Omega) I = 11 V \Rightarrow 11 \Omega I = 11 V$

$I = 1 A$

$(5 \Omega + 6 \Omega) I = 11 V$

$(5 \Omega + 6 \Omega) I = 11 V \Rightarrow 11 \Omega I = 11 V$

$\frac{(5 \Omega + 6 \Omega) I}{I} = 11 V$


$I = 1 A$

$5 \Omega + 6 \Omega = 11 \Omega$

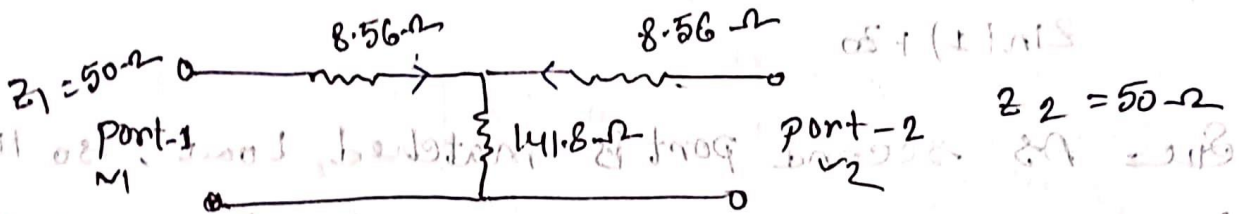Example - 4.4 :-

Find the scattering parameter of the 3dB antenna for circuit shown below

⇒ (Attenuator circuit means:- If we give power input at port - 1 & the output that we get at port two, the power will reduce)



Ans:-

$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

So,

$$V_1^- = S_{11} \times V_1^+ + S_{12} \times V_2^+$$

$$V_2^- = S_{21} \times V_1^+ + S_{22} \times V_2^+$$

$$S_{11} = \frac{V_1^-}{V_1^+} \Big|_{V_2^+ = 0} \quad \left. \begin{array}{l} S_{21} = \frac{V_2^-}{V_1^+} \Big|_{V_2^+ = 0} \\ S_{12} = \frac{V_1^-}{V_2^+} \Big|_{V_1^+ = 0} \quad \left. \begin{array}{l} S_{22} = \frac{V_2^-}{V_2^+} \Big|_{V_1^+ = 0} \end{array} \right\}$$

For S_{11} reflection coefficient of port 1, $v_2^+ = 0$

$$S_{11} = \frac{V_1^-}{V_1^+} \Big|_{v_2^+ = 0}$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Load Impedance Z_L
Input Impedance Z_0


to find S_{11} at port 1, $v_2^+ = 0$

$S_{11} = \Gamma$ (reflection coefficient)

$$S_{11} = \frac{Z_{in}(1) - Z_0}{Z_{in}(1) + Z_0}$$

As second port is matched load, so there is no chance to get any output from port-2

As we matched by 50Ω load of port-2 :-

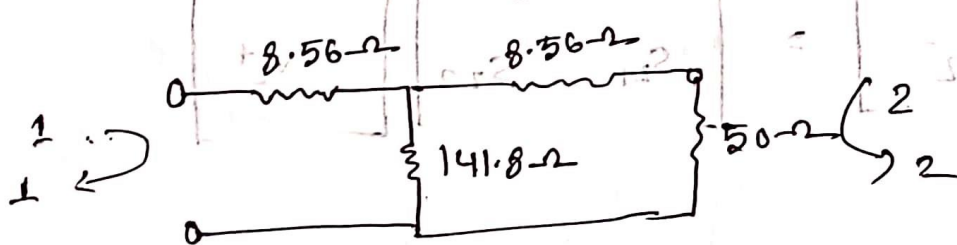

$$Z_{in} = \left\{ (50 + 8.56) \parallel (141.8) \right\} + 8.56$$

$$= \left[58.56 \parallel 141.8 \right] + 8.56$$

$$= 50\Omega$$


$$S_{11} = \frac{50 - 50}{50 + 50} = 0$$

And also $S_{22} = 0$ (Because of the symmetry of the circuit)

Here, we can say that the device is reciprocal.

As from port-1 to port-2 which power will be faced from port-2 to port-1 will face the

same (power) = S_{12}

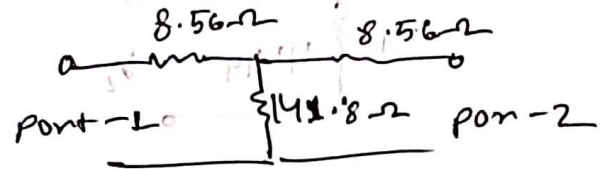


So, $S_{12} = S_{21}$

$$S_{12} = \frac{v_1^-}{v_2^+} \Big|_{v_1^+ = 0} \because v_1 = v_1^+ + v_1^-$$

$$v_1 = v_1^-$$

$$\Rightarrow S_{12} = \frac{v_1}{v_2} \quad \text{and} \quad v_2 = v_2^+ + v_2^-$$
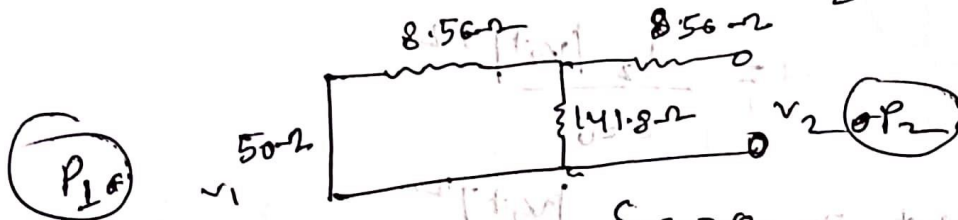
$$v_2^+ = v_2 \quad [\because v_2^- = 0]$$





$S_{22} = 0$

As, $S_{22} = 0$; so, 2nd port is Input दिल 2nd पोर्ट Output পাওয়ার কোন সম্ভাবনা নাই। অর্থাৎ 2nd पोर्टে ইনপুট দিলে 1st पोर्ट থেকে reflected হবে অর্থাৎ সম্ভাবনা নাই।

$$v_2^- = 0$$

→ Quiz P1 → 12

P2 → 13.5

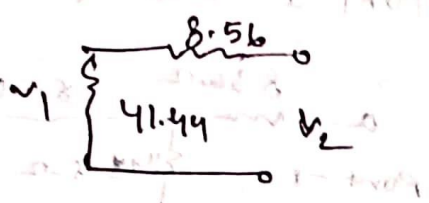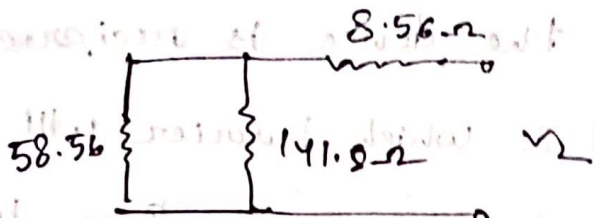

$$v_2 = \left(\frac{41.44}{41.44 + 8.56} \right) \times v_1 \times \frac{50}{50 \times 8.56}$$

$$v_2 = 0.707 v_1$$

Input power $\frac{|v_2^+|^2}{2Z_0}$

Output power $= \frac{|[v_1^-]|^2}{2Z_0}$ $\therefore S_{12} = \frac{v_1^-}{v_2^+}$

$= \frac{|S_{12} \cdot v_2^+|^2}{2Z_0}$ $v_1^- = S_{12} v_2^+$

$= \frac{1/2 |v_2^+|^2}{2Z_0}$

\therefore output power $= \frac{|v_2^+|^2}{4Z_0}$

Output power decreased by 50%

S matrix $= \begin{bmatrix} 0 & 0.707 \\ 0.707 & 0 \end{bmatrix}$

Handwritten signature or mark.

Freq \rightarrow min \rightarrow 1 GHz

max \rightarrow 3 GHz

Time \rightarrow ns \rightarrow Monitors \rightarrow E-Field, H-Field, Far Field

\rightarrow Exp Name

\rightarrow component

\rightarrow Calculation table

$$L = -75$$

$$n = 2.5$$

(fingered tracks)

$$+75$$


$$n = 2.5$$

$n \rightarrow$ Axis \rightarrow 2.5

\rightarrow Result Analysis

\rightarrow Discussion

S-parameter

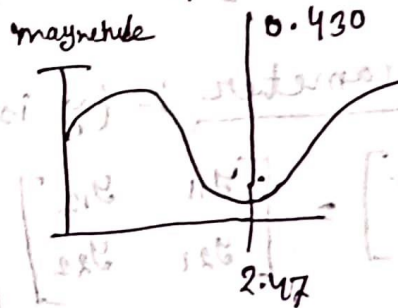

$n = 2.5$

+75	-75
+10	-10

3 GHz design \rightarrow LV \rightarrow 2.472 GHz \rightarrow Reflection Coefficient

(some information about the design)


Loss in metals \rightarrow 2.4 GHz Loss \rightarrow 0.002206

Power Acceptance:

\rightarrow Frequency

0.09

S-Matrix

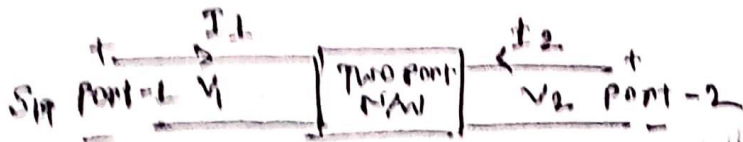

h-parameter:

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$V_1 = h_{11} \cdot I_1 + h_{12} \cdot V_2 \quad \text{--- (1)}$$

$$I_2 = -h_{21} \cdot I_1 + h_{22} \cdot V_2 \quad \text{--- (2)}$$

$$\therefore h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} \quad (\text{short circuit})$$

$$\therefore h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} \quad (\text{open circuit}) \quad [I_{\text{current}}=0]$$

y-parameter: (y is called as admittance)

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$I_1 = y_{11} \cdot V_1 + y_{12} \cdot V_2 \quad \text{--- (1)}$$

$$I_2 = y_{21} \cdot V_1 + y_{22} \cdot V_2 \quad \text{--- (2)}$$

z-parameter: (Represents Information with Impedance)

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


ABCD parameters:-

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Limitation of this params:-

① Equipment is not available to stably measure E/H instead of V/I.

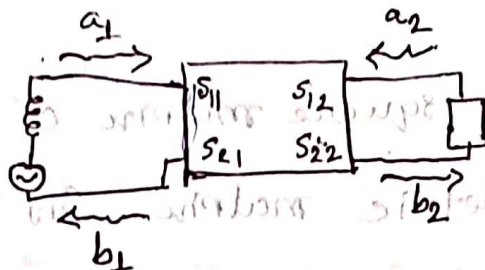② Short circuit & open circuit very difficult to achieve.



S = Reflection coefficient

a = Incident wave

b = Reflected wave

$n \times n$ port device:-

$$\begin{bmatrix} b_1 \\ b_2 \\ \vdots \\ b_n \end{bmatrix} \begin{matrix} (n \times 1) \\ \text{Reflected wave} \end{matrix} = \begin{bmatrix} S_{11} & S_{12} & \dots & S_{1n} \\ S_{21} & S_{22} & \dots & S_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ S_{n1} & S_{n2} & \dots & S_{nn} \end{bmatrix} \begin{matrix} (n \times n) \\ \text{Scattering Matrix} \end{matrix} \begin{bmatrix} a_1 \\ a_2 \\ \vdots \\ a_n \end{bmatrix} \begin{matrix} (n \times 1) \\ \text{Incident waves} \end{matrix}$$

$$\therefore b_1 = S_{11} \cdot a_1 + S_{12} \cdot a_2 + \dots + S_{1n} \cdot a_n$$

$$\therefore b_2 = S_{21} a_1 + S_{22} \cdot a_2 + \dots + S_{2n} \cdot a_n$$

$$\therefore b_n = S_{n1} a_1 + S_{n2} \cdot a_2 + \dots + S_{nn} \cdot a_n$$

a = Input to particular port

b = output from particular port

S_{ij} = scattering coefficient

S_{ij} (Input at i th port & output taken from j th port)

S_{ii} → power reflected back from junction

properties:-

① $[S]$ is always a square matrix of order $n \times n$

② $[S]$ is a symmetric matrix $S_{ij} = S_{ji}$

③ Unitary property / matrix

$$[S] \cdot [S]^* = [I] \rightarrow \text{Identity matrix}$$

Scattering matrix

Complex

Conjugate of $[S]$

$$\begin{bmatrix} S_{11} \\ S_{21} \\ \vdots \\ S_{n1} \end{bmatrix}$$

$$\begin{bmatrix} S_{11}^* & S_{12}^* & \dots & S_{1n}^* \\ S_{21}^* & S_{22}^* & \dots & S_{2n}^* \\ \vdots & \vdots & \ddots & \vdots \\ S_{n1}^* & S_{n2}^* & \dots & S_{nn}^* \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 0 & \dots & 0 \\ 0 & 1 & \dots & 0 \\ \vdots & \vdots & \ddots & \vdots \\ 0 & 0 & \dots & 1 \end{bmatrix}$$

($n \times n$)
($n \times n$)

($n \times n$)
matrix

($n \times n$)
matrix

Example-1:- The S-matrix of a two-port network is

given by,

$$[S] = \begin{bmatrix} 0.2 \angle 0 & 0.9 \angle 90 \\ 0.9 \angle 90 & 0.1 \angle 90 \end{bmatrix}$$

Find given network is lossless & reciprocal.

Reciprocal \Rightarrow Transpose $\begin{bmatrix} \text{Row} \rightarrow \text{Column} \\ \text{Column} \rightarrow \text{Row} \end{bmatrix}^T$

$$[S]^T = \begin{bmatrix} 0.2 \angle 0 & 0.9 \angle 90 \\ 0.9 \angle 90 & 0.1 \angle 90 \end{bmatrix} = [S]$$

As $[S]^T = [S]$ That means give network is reciprocal.

Lossless:- $(\text{Row } 1)^2 + (\text{Row } 2)^2 = 1$ that means lossless

we know,

$$S_{11}^2 + S_{12}^2 + S_{13}^2 + \dots + S_{1n}^2 = 1$$

So, $(0.2)^2 + (0.9)^2 = 0.85 \neq 1$ [That means it is not lossless network. It is lossy network.]

Example-2:-

The S-matrix of a four-port network is given by,

$$[S] = \begin{bmatrix} 0.1 \angle 90 & 0.8 \angle 45 & 0.3 \angle 90 & 0 \\ 0.8 \angle 45 & 0 & 0 & 0.4 \angle 45 \\ 0.3 \angle 45 & 0 & 0 & 0 \\ 0 & 0.4 \angle 45 & 0.6 \angle 45 & 0 \end{bmatrix}$$

Find given network is lossless & reciprocal.

Reciprocal!:-

$$[S]^T = \begin{bmatrix} 0.1290 & 0.8245 & 0.3245 & 0 \\ 0.8245 & 0 & 0 & 0.4245 \\ 0.3245 & 0 & 0 & 0.6245 \\ 0 & 0.4245 & 0.6245 & 0 \end{bmatrix}$$

So, this is S-matrix. So give network is reciprocal

Lossless!:-

For first row, $(0.1)^2 + (0.8)^2 + (0.3)^2 + (0)^2 = 0.74 \neq 1$

So, the entire network is lossy. Not lossless

Ex:-03 The S-matrix of a two-port network is given by

$$[S] = \begin{bmatrix} 0.15 \angle 0 & 0.85 \angle -45 \\ 0.85 \angle 45 & 0.2 \angle 0 \end{bmatrix}$$

- Find, ① Network is reciprocal
- ② Network is lossless
- ③ If port 2 is terminated with matched load, find return loss at port-1.
- ④ If port 2 is terminated with short circuit, find return loss at port-1.

Ans:- Reciprocal

$$[S]^T = \begin{bmatrix} 0.15 \angle 0 & 0.85 \angle 45 \\ 0.85 \angle -45 & 0.2 \angle 0 \end{bmatrix} \neq [S]$$

That means it is not reciprocal

(4.11 & 4.22)

(ii) R. Lossless

$$(0.15)^2 + (0.85)^2 = 0.745 \neq 1$$

So, this is lossy network

(iii)

Reflection coefficient, $r_1 = \frac{b_1}{a_1}$

Return Loss, R.L = $-20 \log |r_1|$

For two port networks,

$b_1 = a_1 S_{11} + a_2 S_{12}$ (i)

$b_2 = a_1 S_{21} + a_2 S_{22}$ (ii)

If port 2 is terminated $a_2 = 0$

$b_1 = a_1 S_{11}$

$\therefore S_{11} = \frac{b_1}{a_1} = r_1$

Again from matrix, $S_{11} = 0.15$

\therefore return loss = $-20 \log |0.15|$
 $= 16.47 \text{ dB}$

(iv) When you terminate port-2 with short circuit,

$a_2 = -b_2$

$\therefore b_1 = a_1 S_{11} + a_2 S_{12}$

$\therefore b_2 = a_1 S_{21} + a_2 S_{22} \Rightarrow b_2 (1 + S_{22}) = a_1 S_{21}$

$\therefore b_2 = \frac{a_1 S_{21}}{1 + S_{22}}$

So,

$$\Rightarrow b_1 = a_1 s_{11} - \cancel{a_2} \left(\frac{s_{12} \cdot s_{21}}{1 + s_{22}} \right)$$

$$\therefore \frac{b_1}{a_1} = s_{11} - \frac{s_{12} \cdot s_{21}}{1 + s_{22}}$$

$$= 0.15 - \frac{0.85 \times 0.85}{1 + 0.2} = 0.15 - 0.625 = -0.475$$

$$= -0.475 = \rho_1$$

$$\rightarrow \text{Return Loss, } RL = -20 \log |\rho_1| = -20 \log |0.475|$$

$$= 6.93 \text{ dB}$$

Book ex-01 (1.2)

Consider a series RLC circuit with a current I . Calculate the power lost & the stored electric & magnetic energies,

and show that the input impedance can be expressed as a

certain three-port network is lossless & reciprocal, & has $s_{13} = s_{23}$

& $s_{11} = s_{22}$. Show that if port-2 is terminated in a reactance Z_0

that the other two ports (say port-1 & port-2) are decoupled

(no power flow from port-1 to port-2, or from port-2 to port-1)



$\rho_1 = 0.475$, return loss 6.93 dB

$RL = -20 \log |0.475| = 6.93 \text{ dB}$

$RL = 6.93 \text{ dB}$

When port-2 is terminated with short circuit (v)

$$s_{22} = \rho_2$$

$$s_{11} = \rho_1 = 0.475$$

$$s_{12} = s_{21} = \rho_{12} = 0.475$$

$$s_{13} = s_{23} = \rho_{13} = 0$$

Theory



Q) Need of Network Analysis:-


- TO design & analyze Microwave circuit
- TO characterize Microwave devices
- TO measure the performance of MW devices
- TO troubleshoot MW problems.
- TO develop new microwave technologies.
- Signal Integrity
- Power Transfer
- Frequency Domain Analysis.
 - Filter Design
 - Antenna tuning.
 - System Stability & Reliability.

Q) (i) Although there are Z & y matrices available, why do we need S -matrix?

(ii) Need of S -Matrix: -

Ans:- Z & y matrices are used in high frequencies to calculate while the S -matrix is used to calculate the microwave analysis. S -matrix is also used to determine the reflection co-efficient & transmission gain from both sides of a two port network. So, we need S -matrix.

* Derive ABCD Matrix:-

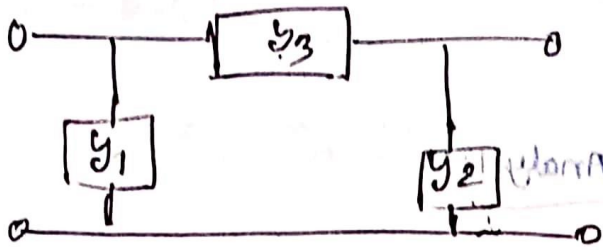

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \frac{-y_{22}}{y_{21}} & \frac{-1}{y_{21}} \\ \frac{-y_{12}}{y_{21}} & \frac{-y_{11}}{y_{21}} \end{bmatrix}$$

$$[-y_{12} = y_{12}, y_{21} = -y_{11}, y_{22}]$$

$$A = \frac{-y_{22}}{y_{21}} = \frac{-(y_2 + y_3)}{-y_3} = 1 + \frac{y_2}{y_3}$$

$$B = \frac{-1}{y_{21}} = \frac{-1}{-y_3} = \frac{1}{y_3}$$

$$C = \frac{-y_{12}}{y_{21}} = \frac{y_{12} \cdot y_{21} - y_{11} \cdot y_{22}}{y_{21}^2}$$

$$= \frac{(-y_3)(-y_3) - (y_1 + y_3)(y_2 + y_3)}{-y_3}$$

$$= \frac{y_1 y_2 + y_1 y_3 + y_2 y_3}{-y_3}$$

$$= \frac{y_3 \left(\frac{y_1 y_2}{y_3} + y_1 + y_2 \right)}{-y_3}$$

$$= -\left(\frac{y_1 y_2}{y_3} + y_1 + y_2 \right)$$

$$= y_1 + y_2 + \frac{y_1 y_2}{y_3}$$

$$D = \frac{-y_{11}}{y_{21}} = \frac{-(y_1 + y_3)}{-y_3} = 1 + \frac{y_1}{y_3}$$

Derive ABCD matrix for Fig-1



$$\Rightarrow \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

Then, $A = \frac{V_1}{V_2} \Big|_{I_2=0} = 0$

Which indicates that A is found by applying a voltage V_1 at port-1, and measuring the open circuit voltage V_2 at port-2, thus $0 \cdot A = 1$

Then, $B = \frac{V_1}{I_2} \Big|_{V_2=0} = \frac{V_1}{V_1/2} = 2$

$C = \frac{I_1}{V_2} \Big|_{I_2=0} = 0$

$D = \frac{I_1}{I_2} \Big|_{V_2=0} = \frac{I_1}{I_1} = 1$

What are the meaning of ABCD? And how to

calculate this?

\Rightarrow ABCD matrix usually refers to a mathematical representation used in electrical engineering such as two port networks.

The ABCD matrix is powerful in the context of how circuit analysis & transmission line applications while representing & when dealing with multiport networks.

A-Transmission (Forward voltage gain):-

B-Transmission (Reverse voltage gain)

C-Transmission (Forward current gain)

D-Transmission (Reverse current gain)

$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$ → This is how ABCD matrix looks like.

To calculate this we use circuit analysis techniques.

The values can depend on the specific characteristics within the network, such as resistors, capacitors & inductors.

In the context of transmission lines, the ABCD matrix is determined by the characteristic impedance & propagation constant of the TL.

☐ Why we need ABCD matrix while we have S-matrix?

⇒ Both are important. And have ~~use~~ usage.

The use of these ~~are~~ depends on the specific characteristics of the electrical network & the nature of the analysis you are performing. The ABCD matrix is often preferred for simpler circuit analysis & transmission line applications while the S-matrix is powerful in the context of MW Engineering & when dealing with multi-port networks.

Q) How to calculate S-Matrix value? S, i, j equation meaning?

⇒ S-matrix used to describe the relationship between the incident & reflected waves at each port OF a linear network.

$$[S] = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}$$

$$[S] = \begin{bmatrix} S_{11} & S_{12} & \dots & S_{1n} \\ S_{21} & S_{22} & \dots & S_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ S_{n1} & S_{n2} & \dots & S_{nn} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_n \end{bmatrix}$$

S_{ij} ⇒ Here i means where incident wave originates.

Here j, means where the wave is reflected.

Example - S_{12} → Here Input is at port 1 & Output is at port 2.

☐ Reciprocal, Lossless, Matched at all ports & what does that mean?

=> Reciprocal! - This device transmits power in both directions equally.

$$[S] = [S]^T$$

Row - column change \rightarrow same element

Reciprocal $S_{12} = S_{21}$ $S_{13} = S_{31}$...

$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} = \begin{bmatrix} S_{11} & S_{21} \\ S_{12} & S_{22} \end{bmatrix}$$

Lossless! - Lossless means the device does not dissipate any power.

$(\text{Row})^2 = 1$ if all values of a row in the matrix $\neq 1$ then it will be a lossy device.

Matched! - The impedance of each port is equal to the characteristic impedance of the transmission line that is connecting the device to the rest of the system.

Antennas

① What is Antenna? Modes of Antenna

⇒ The thing which converts Radio Frequency into Electrical Energy & converts Electrical Energy into Radio Frequency. It also can transmit & Receive signals.

Mode of Antenna:-

(1) TEM Mode (Transverse Electromagnetic Mode)

⇒ Both electric & magnetic fields are transverse to the direction of propagation.

(2) TE Mode (Transverse Electric Mode) & TM mode

(3) HE Mode (Hybrid Electric Mode) (Transverse magnetic)

(4) Resonant Modes

(5) Higher-order Modes.

② Losses in an Antenna:-

(i) Conductor dielectric loss:- If there are difference in between two antennas that means it is dielectric loss.

(ii) Impedance mismatch Loss:- Depends on the design. Antenna \neq impedance & Transmission Line \neq impedance mismatch.

(iii) Material Loss:- It is material based thing, so any loss in material will create this.

(iv) Polarization mismatch loss:- when the polarization of the transmitted & received signals does not match.

(v) propagation & Atmospheric losses.

(vi) Ground & Environmental absorption.

③ Antenna efficiency, Total efficiency, radiation efficiency.

⇒ Antenna efficiency:- Measure of how well an antenna converts the input power from the transmitter into radiated electromagnetic waves.

$$\epsilon_0 = \epsilon_r \epsilon_c \epsilon_d$$

ϵ_0 = total efficiency

ϵ_r = reflection (mismatch) efficiency

ϵ_c = conduction efficiency

ϵ_d = dielectric efficiency

Total efficiency:-

It includes not only the radiation efficiency but also considers the losses in the entire communication system.

Radiation efficiency:- Specifically focuses on the losses associated with the radiation process.

A measure of how effectively the antenna radiates electromagnetic waves, & often expressed as a percentage.

- 4) works of Antenna:- 3 works:-
- (1) Wireless Communication
 - (i) Free space wave to direction (user)
 - (ii) wave to radiate
 - (2) cellular Networks :- Antennas used in base station
 - (iii) Wi-Fi Networks :- Antennas are employed in routers.
 - (iii) Bluetooth & Zigbee
 - (2) Broadcasting
 - (i) TV & radio
 - (3) Satellite Communication :-
 - (i) Ground Station
 - (4) Radar Systems :-
 - (i) Air Traffic Control Radar.
 - (ii) Automotive Radar
 - (5) Radio Frequency Identification
 - (6) Wireless Sensor Networks.

5) Antennas parameters value depends on the application

⇒ Depends on the application. Some key parameters are given below :-

(1) Radiation pattern :- mathematical function or graphical representation of the radiation properties of an antenna describes how it distributes radio waves in space. 3 types

- (2) Gain
- (i) Isotropic Antenna :- সর্বদিকের বিকিরণ সমান
 - (ii) Omnidirection Antenna :- x, y সমান, z axis এ মাত্র একটি দিকের বিকিরণ।

(iii) Directional pattern! - ଏକ Direction ଏ ଡାଲି ବା ଡିରେକ୍ସନାଲିଟି ।
ଏହା ଡାଲି କାନ୍ଧ ଗଠେ ।

2) Gain: Determines the antenna's ability to focus or concentrate its radiation in a particular direction.

There are two types:- High distance! - use in Satellite
Low " :- Used for local wireless.

(3) polarization! - Antennas can be polarized vertically, horizontally, circularly etc.

The polarization of antenna should match the polarization of signals.

Example! - Linear polarization is common in terrestrial wireless communication, circular polarization is used in satellite communication. (Importance)



(4) Impedance! - Antenna impedance should match the impedance of TL & to minimize the signal loss.

(7) Half power beam width / Antenna beam width:-
(HPBW)

Antenna beam width is an angular beam width in degree measure on radiation pattern, between the points where radiated power has fallen half. If it is directional then there will be a major lobe. And the lobe of opposite part (180° opposite) back lobe.

And all lobe except major lobe are minor lobe.

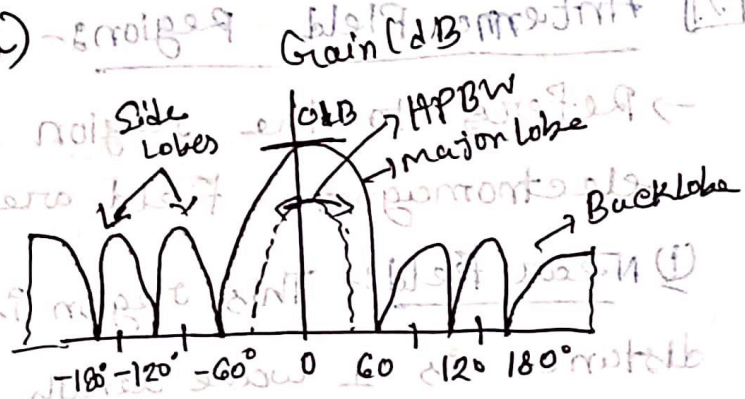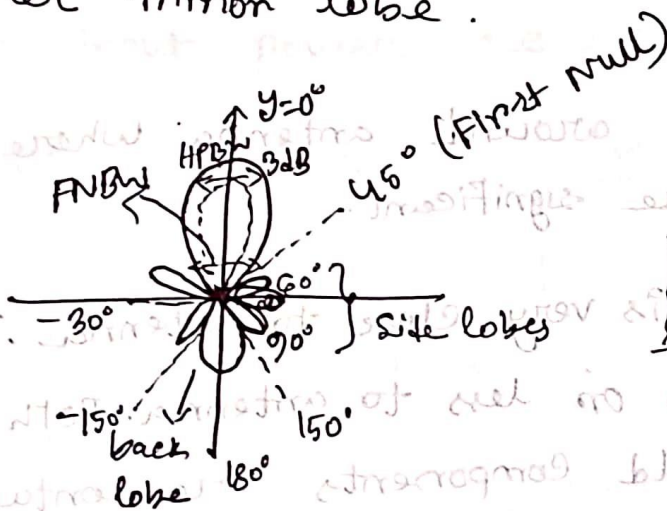And the lobe inside the minor lobe which carries the most power is called as side lobe. Side lobe needs to be reduced to forget all other minor lobe.



(8) Radiation Lobes / Antenna Lobes:-

4 types:-

(1) Main Lobe:- primary & most significant lobe. It contains highest level of radiated energy.

(2) Minor Lobe:- Any radiation lobe other than the main lobe.

(3) Side Lobe:- Additional lobes in the radiation pattern that are not as strong as main lobe. These can be uncoupled for some application.

(4) Back lobe:- It is situated in the opposite (180° opposite) of the major lobe. It is called as back lobe.

(9) Antenna Field Regions:-

→ Refers to the region around antenna where its electromagnetic field are significant.

(i) Near Field:- This region is very close to antenna. The distance is ≤ 1 wave length or less to antenna. Both electric & magnetic field components are contained.

(ii) Radiating Near Field:- Further from near but closer than far field. Distance is 2 wavelength from antenna.

(iii) Far Field:- Greater than few wavelength from antenna. The field components are essentially transverse.

(10) Directivity :-

Ratio of radiation power/intensity in a given direction from the antenna to the radiation intensity avg over all direction.

$$D = \frac{U_{\text{given direction}}}{U_{\text{avg overall direction}}}$$

Average Radiation intensity,

$$U_{\text{avg}} = \frac{P_{\text{rad}}}{4\pi}$$

$$\text{Directivity, } D = \frac{4\pi U}{P_{\text{rad}}}$$

$$\text{max directivity ; } D_{\text{max}} = \frac{4\pi U_{\text{max}}}{P_{\text{rad}}}$$

(11) Antenna efficiency :-

Ratio of the radiated power of the antenna to the input power accepted by antenna.

$$\text{Antenna efficiency} = \frac{\text{Radiated power}}{\text{Input power}} \times 100\%$$

$$\text{Total efficiency, } e_0 = e_c e_d e_r$$

$$\text{Radiation efficiency, } e_r = \frac{e_0}{e_c e_d}$$

(12) Gain of an Antenna :-

(गुणक गुणक)

$$\text{Efficiency} = \frac{\text{Gain}}{\text{Directivity}}$$

(13) Difference between gain & directivity:

	Gain	Directivity
Definition	measure of an antenna's ability of how well the antenna converts input power into radio waves headed in a specific direction.	→ Ability of an antenna to focus energy in a particular direction.
units	Decibels over Isotropic (dBi)	Unitless
Relationship	Gain = Efficiency × Directivity	Directivity is a component of gain.
	Gain is used in characterizing the effective range.	point to point communication on star network
	Ex:- parabolic dish antenna	Ex:- patch antenna

(14) Antenna Bw Classification:-

- Narrow Band
- Less than 3 MHz
 - High Gain
 - narrow Beam width
 - Vertical / Horizontal polarization
 - usage in low traffic.

(2) BroadBand:-

- 3 to 30 D MHz
- Medium gain
- Medium beam width
- vertical & horizontal polarization
- usage medium

(3) Widthband:-

- 300 MHz to 3 GHz
- Low gain
- wide beam width
- vertical / horizontal polarization
- High

(4) Ultra-wide Band:-

- Greater than 3 GHz
- Gain very low
- Ultra wide beam width
- vertical / horizontal
- very High

pdf:- Micro tubes

- 7(13.2) → multi cavity
- 13.3 (Reflex kilestone)
- 5 no. page (Transmit ~~point~~)
- ~~Reflex~~ Magnatron (13.4)
- TWT Foundations

$$S_{out} = S_{in} + S_{in} \cdot \frac{1}{d} = (S) \cdot \frac{1}{d}$$

Time point

$$S_{out} = \frac{S_{in}}{d} = (S) \cdot \frac{1}{d}$$